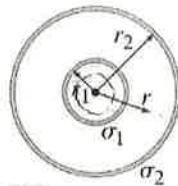


## Problem 1 (33 Points)

Two thin concentric spherical shells of radii  $r_1$  and  $r_2$  ( $r_1 < r_2$ ) contain uniform surface charge densities  $\sigma_1$  and  $\sigma_2$  respectively (see Fig. below).




Gauss's Law  $\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{en}}}{\epsilon_0}$  (3)

Determine the electric field for

(a)  $0 < r < r_1$ ,  $\oint \vec{E} \cdot d\vec{A} = \int \epsilon_0 dA \cos 0 =$

$$\oint \epsilon_0 dA \cos 0 = \epsilon_0 \oint dA = \epsilon_0 A = \epsilon_0 (4\pi r^2)$$

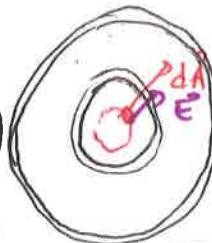(10)  $Q_{\text{en}} = 0$  inside  $\Rightarrow \oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{en}}}{\epsilon_0} = \frac{0}{\epsilon_0} \Rightarrow E = 0$




(b)  $r_1 < r < r_2$ ,

$$\oint \vec{E} \cdot d\vec{A} = \oint \epsilon_0 dA \cos 0 = \epsilon_0 \oint dA = \epsilon_0 A = \epsilon_0 (4\pi r^2)$$

$$Q_{\text{en}} = \sigma_1 A_1 = \sigma_1 (4\pi r_1^2)$$

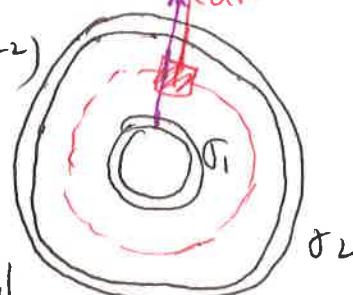(10)  $\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{en}}}{\epsilon_0} = \frac{\sigma_1 (4\pi r_1^2)}{\epsilon_0} \Rightarrow E = \frac{\sigma_1}{\epsilon_0} \frac{r_1^2}{r^2}$



and (c)  $r > r_2$ .

$$\oint \vec{E} \cdot d\vec{A} \text{ stay the same} = \epsilon_0 (4\pi r^2)$$


$$Q_{\text{en}} = \sigma_1 A_1 + \sigma_2 A_2$$

(10)  $Q_{\text{en}} = \sigma_1 (4\pi r_1^2) + \sigma_2 (4\pi r_2^2)$

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{en}}}{\epsilon_0}$$


$$\epsilon_0 (4\pi r^2) = \frac{1}{\epsilon_0} (\sigma_1 (4\pi r_1^2) + \sigma_2 (4\pi r_2^2))$$
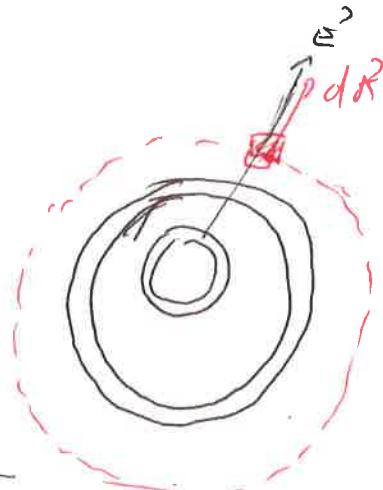
$$\epsilon_0 = \frac{\sigma_1 r_1^2 + \sigma_2 r_2^2}{\epsilon_0 r^2}$$



## Problem 2 (34 Points)

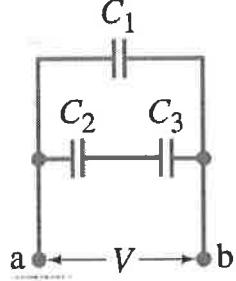(a) Determine the equivalent capacitance of the circuit shown in figure below.



$$C_2 \parallel C_3 \rightarrow \frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{C_3 + C_2}{C_2 C_3}$$

$$\Rightarrow C_{23} = \frac{C_2 C_3}{C_3 + C_2}$$

(16)

$$C_{eq} = C_1 + \frac{C_2 C_3}{C_3 + C_2}$$

(b) If  $C_1 = C_2 = 2C_3 = 24\mu F$ , how much charge is stored on each capacitor when  $V = 35.0 V$ ?

$$V_{ab} = V_{C_2 C_3} = V_{C_1} = 35.0 V$$

$$Q_1 = C_1 V_{C_1} = (24 \times 10^{-6} F)(35.0 V) = 8.4 \times 10^{-4} C$$

$$Q_{23} = C_{23} V_{C_2 C_3}$$

$$C_{23} = \frac{C_2 C_3}{C_3 + C_2}$$

$$C_3 = \frac{1}{2} C_2 = \frac{1}{2} C \quad (18)$$

$$C_{23} = \frac{C (\frac{1}{2} C)}{\frac{1}{2} C + C} = \frac{\frac{1}{2} C^2}{\frac{1}{2} C + \frac{2}{2} C} = \frac{\frac{1}{2} C^2}{\frac{3}{2} C} = \frac{C}{3}$$

$$Q_{23} = \frac{C}{3} V_{C_2 C_3} = \frac{24 \times 10^{-6} F}{3} (35.0 V) = 2.80 \times 10^{-4} C$$

$= Q_2 = Q_3$  (same charge ( $C_2 \parallel C_3$  in series))

**Problem 3 (33 Points)**

An extension cord made of two wires of diameter 0.129 cm and of length 2.7 m is connected to an electric heater which draws 15.0 A on a 120-V line. The resistivity of the copper is  $1.68 \times 10^{-8} \Omega \cdot m$ .

How much power is dissipated in the cord?

$$V = 120 \text{ V}$$

$$I = 15.0 \text{ A}$$

$$l = 2.7 \text{ m}$$

$$d = 0.129 \text{ cm}$$

$$\rho = 1.68 \times 10^{-8} \Omega \cdot \text{m}$$

$$P = I^2 R \quad (5)$$

$$R = \frac{\rho l}{A} \quad (5) \qquad A = \pi r^2 = \pi \left(\frac{d}{2}\right)^2 = \pi \frac{d^2}{4} \quad (6)$$

$$P = I^2 \frac{\rho l}{A} = I^2 \frac{\rho l}{\pi \frac{d^2}{4}} = \frac{4 I^2 \rho l}{\pi d^2} \quad (8)$$

$$P = \frac{4 (15.0 \text{ A})^2 (1.68 \times 10^{-8} \Omega \cdot \text{m}) (5.4 \text{ m})}{\pi (0.129 \times 10^{-2} \text{ m})^2} = 15.62 \text{ W}$$