

$$97 + 5 = \frac{102}{10}$$

I. Select the correct answer for the following multiple choice questions and write your answer in the line next to the question number.

e 1. What is the SI unit for *electromotive force*?
 a. N b. A c. W d. J e. V f. Ω

c 2. Identify the smallest energy unit below:
 a. joule b. Btu c. eV d. food Calorie e. calorie

a 3. An appliance is connected to a 120-volt outlet and it draws a current of 0.25 A.
 What is the power of the appliance?
 a. 30 W b. 60 W c. 80 W d. 120 W e. 240 W

$I = 0.25A$
 $V = 120V$
 $P = IV$
 $P = (0.25 \times 120V)$
 $P =$

C 4. Which one of the following biomedical application deals with the brain?
 a. EGK b. EKG c. EEG d. ERG e. CEG

B 5. In a common household circuit, devices are connected in
 A. Series B. Parallel

d 6. A metal wire of length L and cross-sectional area A , has a resistance R . What will be the resistance of the same material and length but twice the radius?
 a. $4R$ b. $2R$ c. R d. $\frac{1}{2}R$ e. $\frac{1}{4}R$


$R \propto \frac{1}{A} \rightarrow R \propto \frac{1}{(\frac{1}{2}r)^2} = \frac{1}{\frac{1}{4}r^2}$

b 7. Which one of the following is placed between capacitor plates to increase the capacitance?
 a. Conductor b. Dielectric c. Resistance d. Semiconductor

a, d, e 8. Identify the scalars among the quantities below? (Multiple Answers)
 a. Electric potential b. Electric field c. Electric force
 d. Electric energy e. Electric power

a 9. What is the charge in the $3 \mu F$ capacitor for the capacitor circuit shown below?

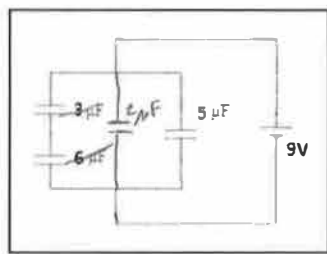- a. $18 \mu C$
- b. $27 \mu C$
- c. $45 \mu C$
- d. $54 \mu C$
- e. $63 \mu C$




$V_T = 9.0V$
 $C_T = 7 \mu F$
 $Q_T = C_T V_T = (7 \mu F) \times (9.0V) = 63 \mu C$
 $Q_{3,6} = C_{3,6} \times 9.0V = 18 \mu C$
 (3 μF)

$V_T = 8.0V$
 $R_T = 10 \Omega$
 $I_T = \frac{V_T}{R_T} = \frac{8.0V}{10 \Omega} = 0.8A$
 $V_s =$

C 10. What is the voltage across the 7Ω resistor in the circuit shown below?

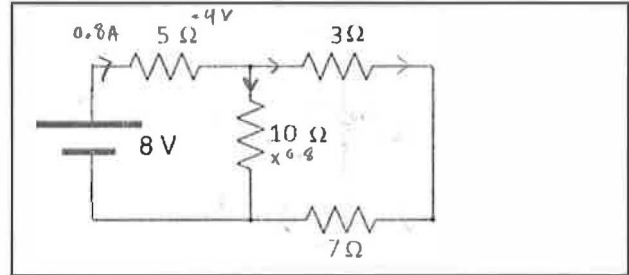- a. 1.2 V b. 2.0 V
- c. 2.8 V d. 6.0 V e. 8.0 V




Series
 $V = V_A + V_B + V_C$

11-12) A light bulb is connected to a battery as shown below.

- b. 11. What is the direction of the current flow?
 a. 12. What is the direction of the electron flow?

Answers for 11 & 12

- a. Clockwise b. Counterclockwise

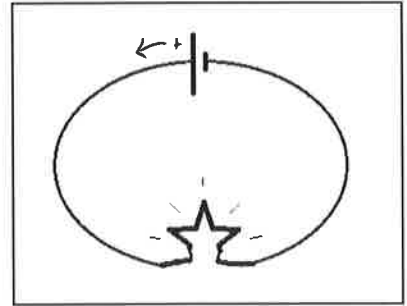

End of MC questions-----

II. Consider the circuit shown in the right.


- a. Show the direction of current for the circuit shown, in the circuit?
 clockwise
- b. Determine the magnitude of the current for the circuit shown?

$$V_T = 30.0V - 10.0V = 20.0V$$

$$R_T = 52 \Omega$$

$$I = \frac{V_T}{R_T} = \frac{20.0V}{52.0\Omega}$$

$$0.38 \text{ A}$$

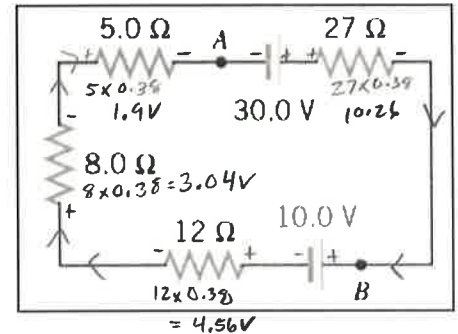

- c. Determine $V_A - V_B$:

$$V_A + 30.0V - 10.26V = V_B$$

$$V_A - V_B = -19.74V$$

III. Estimate the cost of electricity for operating a clothes iron which consumes 4.5 A of current when plugged in a 120-V outlet. It is used 15 minutes a day for 20 days a month for 1 year. Assume a cost of 14 cents per kWh.

$$4.5A \times 120V = 540W \rightarrow .540kW$$

$$(0.540kW) \times \frac{5 \text{ hrs}}{\text{month}} \times 12 \text{ months} \times \$0.14 = \$4.54$$

IV. An evacuated tube uses an accelerating voltage of 48.4 kV to accelerate electrons to hit a copper plate and produce x rays. Non-relativistically, what would be the maximum speed of these electrons? [$m_e = 9.11 \times 10^{-31} \text{kg}$, $|Q_e| = 1.6 \times 10^{-19} \text{C}$]

$$KE = \frac{1}{2}mv^2$$

$$\text{Voltage} = V = \frac{EPE}{Q}$$

$$(48.4 \times 10^3 V) \times (1.6 \times 10^{-19} C) = 7.7 \times 10^{-15} J$$

$$\frac{1}{2}mv^2 = EPE$$

$$\sqrt{\frac{2EPE}{m}} = v = \sqrt{\frac{2 \times (7.7 \times 10^{-15})}{(9.11 \times 10^{-31})}} = 1.3 \times 10^8 \text{ m/s}$$

nC x —


V. At a distance r from a point charge Q , the electric potential, V is given by: $V = k \frac{Q}{r}$.

Four point charges lie in a Cartesian coordinate system as follows: $+6\text{nC}$ at $(-1\text{ m}, 0)$, $+5\text{nC}$ at $(0, 0)$, $+3\text{nC}$ at $(2\text{ m}, 0)$, and -4nC at $(0, 3\text{ m})$. Find the net electric potential at $(2\text{ m}, 3\text{ m})$. Coulomb constant $k = 9 \times 10^9$ (SI), $n = 10^{-9}$.



$$V_T = \left[k \frac{6 \times 10^{-9} \text{ C}}{4.24 \text{ m}} \right] + \left[k \frac{5 \times 10^{-9} \text{ C}}{3.6 \text{ m}} \right] + \left[k \frac{3 \times 10^{-9} \text{ C}}{3 \text{ m}} \right] + \left[k \frac{-4 \times 10^{-9} \text{ C}}{2 \text{ m}} \right]$$

$$V_T = [12.7 \text{ V}] + [12.5 \text{ V}] + [9 \text{ V}] + [-18 \text{ V}]$$

$$V_T = 16.2 \text{ V}$$

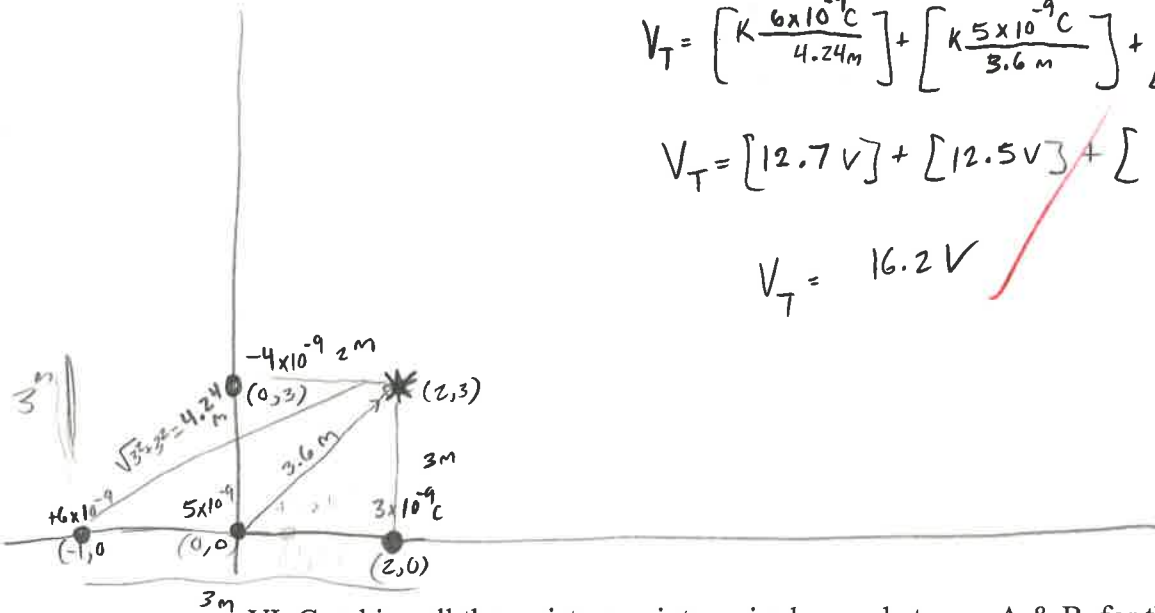

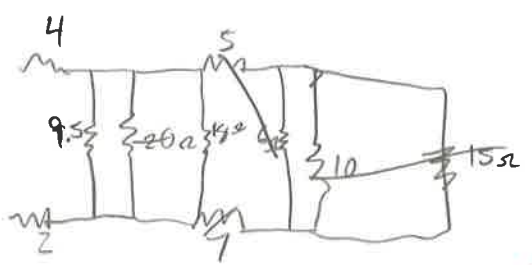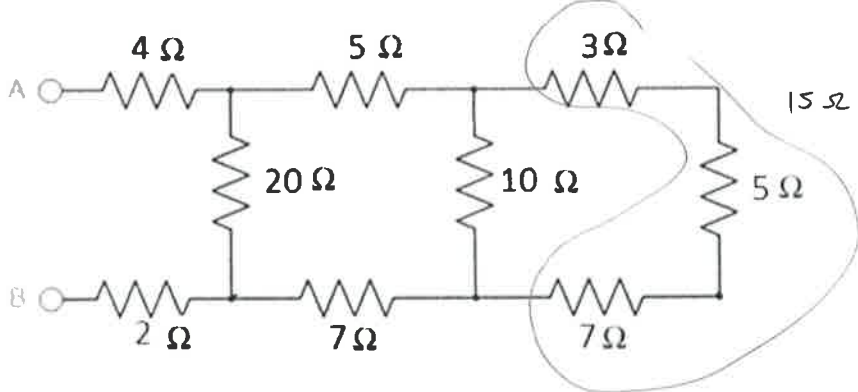
VI. Combine all the resistances into a single one, between A & B, for the circuit shown:



VII. Kirchhoff's Rules.

For the circuit shown:

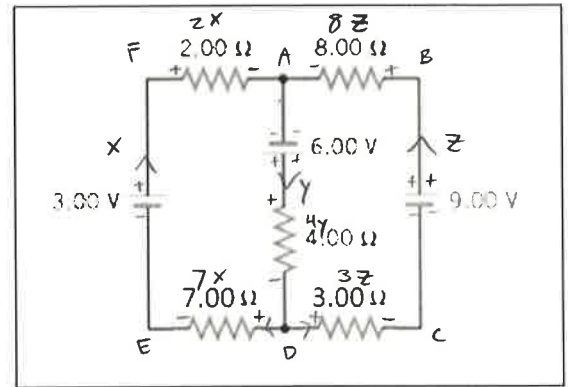1. Assign three unknown currents.
2. Identify the low and high potentials for the resistors and batteries.
3. Write down the potential differences across the resistors in terms of the assigned currents and the given resistance values.
4. Write down the junction rule equation using the assigned currents.



$$X + Z = Y$$

5. Write down the loop rule equation, for the left loop.

ADEFA Rise = Drops

$$6.0 + 3.0 = 4y + 7x + 2x \rightarrow 9.0 = 9x + 4y$$

6. Write down the loop rule equation, for the right loop.

[No need to solve the simultaneous equations]


ABCD A Rise = Drops

$$8.0z + 3.0z + 4y = 9.00 + 6.00 \rightarrow 11z + 4y = 15.00$$

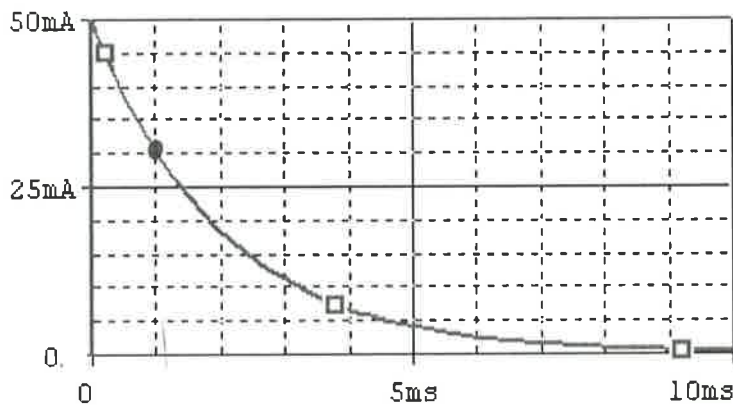VIII. RC circuits: Time constant $\tau = RC$,

$$I = I_0 e^{-\frac{t}{RC}}$$

The variation of the Current as a function of time is shown below for an RC circuit.



Time

1. Read the current at $t = 0$? $50 \text{ mA} = 50 \times 10^{-3} \text{ A}$

2. Read the current at $t = 1 \text{ ms}$? $30 \text{ mA} = 30 \times 10^{-3} \text{ A}$

3. Calculate the time constant using $I = I_0 e^{-\frac{t}{RC}}$.

$$(30 \times 10^{-3}) = (50 \times 10^{-3}) e^{-\frac{(1.00 \times 10^{-3} \text{ s})}{RC}} \rightarrow \ln(0.6) = \left(e^{-\frac{t}{RC}}\right)^{\ln}$$

$$-0.51 = -\frac{1.00 \times 10^{-3}}{RC}$$

$$\rightarrow RC = 0.00196 \text{ s}$$

$$= 1.96 \text{ ms}$$