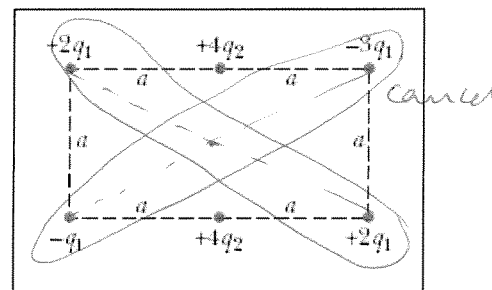


$V = \frac{kq}{r}$      $P = iv = v^2/R = i^2R$     Ohm's law:  $v = iR$      $A_{circle} = \pi r^2$      $R = \rho \frac{L}{A}$

1. In the figure charges are located along the perimeter of a rectangle

of sides  $a$  and  $2a$ . What is the electric potential at the center of the rectangle? ( $a = 10$  cm,  $q_1 = 3 \mu\text{C}$ , and  $q_2 = 5 \mu\text{C}$ )



$$\frac{k \cdot 4q_2}{a/2} + \frac{k \cdot 4q_2}{a/2} = \frac{8kq_2}{a} + \frac{8kq_2}{a} = \frac{16kq_2}{a} = \frac{16 \times 9 \times 10^9 \times 5 \times 10^{-6}}{6 \times 10^{-2}} = 7.20 \times 10^6 \text{ volt}$$

2. A 240 W incandescent light bulb is plugged into a standard 120 V outlet. Assume electrical energy costs US\$ 0.08/kW · h.

(a) How much does it cost in dollars per 31-day month to leave the light turned on 1 hour per day?

(b) What is the resistance of the bulb?

(c) What is the current in the bulb?


(a)  $240 \text{ W} \rightarrow 0.240 \text{ kW}$   
 $31 \text{ days}, 1 \text{ h/day} \rightarrow 31 \text{ h}$

$0.240 \times 31 \text{ kWh} = 7.44 \text{ kWh} \rightarrow \text{Cost} = \frac{\$}{\text{kWh}} \times 7.44 = \frac{\$}{\text{kWh}} \times 0.59 \approx \frac{\$}{\text{kWh}} \times 60$

(c)  $i = \frac{P}{V} = \frac{240}{120} = 2 \text{ A}$

(b)  $R = \frac{V}{i} = \frac{120}{2} = 60 \Omega$

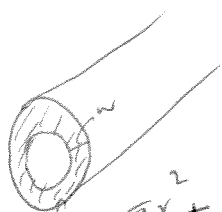3. Suppose a kite string of radius 2.00 mm extends directly upward by 0.800 km and is coated with a 0.500 mm layer of water having resistivity  $150 \Omega \cdot \text{m}$ . If the potential difference between the two ends of the string is 160 MV, what is the current through the water layer?



$A = \pi r^2 + \pi (r+w)^2$   
 $A = \pi (2.5 \times 10^{-3})^2 + \pi (2 \times 10^{-3})^2$   
 $A = 7.07 \times 10^{-6} \text{ m}^2$

$R = \rho \frac{L}{A} = \frac{150 \times 0.8 \times 1000}{7.07 \times 10^{-6}} = 1.7 \times 10^{10} \Omega$

$i = \frac{V}{R} = \frac{160 \times 10^6}{1.7 \times 10^{10}} = 9.4 \text{ mA}$

## Capacitor


Charge:  $q = CV$ ,

Stored energy:  $U = \frac{q^2}{2C} = \frac{1}{2}CV^2$ ,  $C = \frac{K\epsilon_0 A}{d}$


$C_{eq} = \sum_{j=1}^n C_j$  ( $n$  capacitors in parallel)

and  $\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$  ( $n$  capacitors in series).

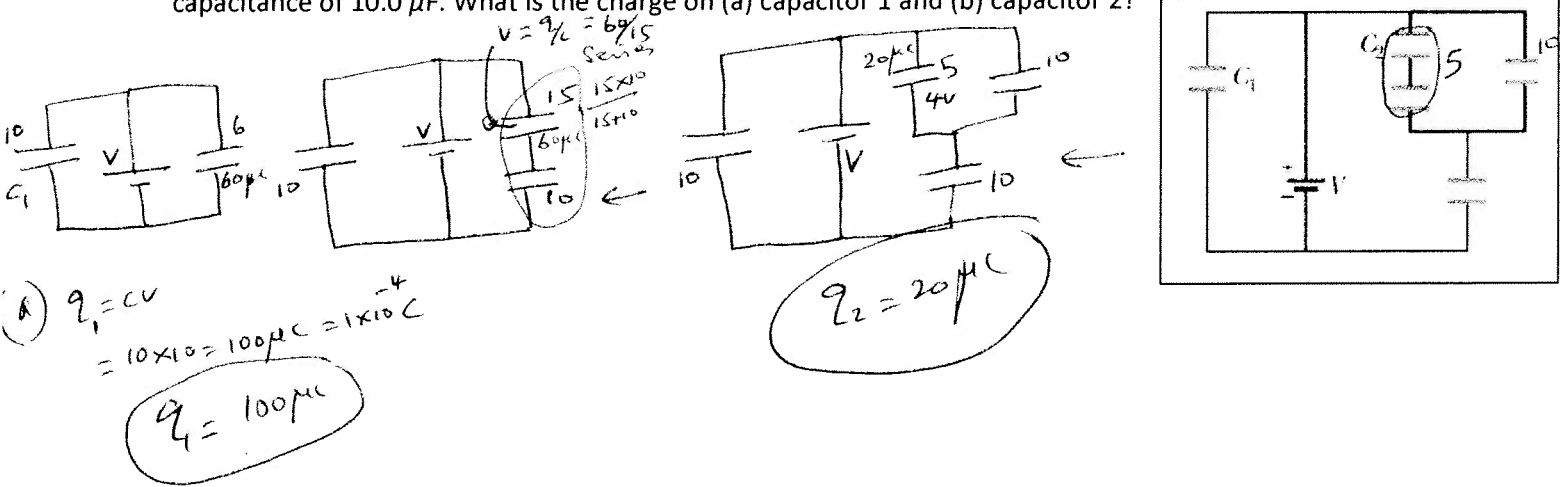4. In the Figure, the battery has a potential difference of  $V = 10.0$  V and the five capacitors each have a capacitance of  $10.0 \mu\text{F}$ . What is the charge on (a) capacitor 1 and (b) capacitor 2?



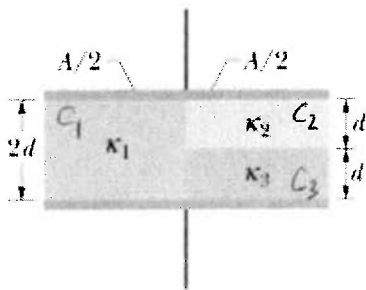5. Figure below shows a parallel-plate capacitor of plate area  $A = 10.5 \text{ cm}^2$  and plate separation  $2d = 7.12 \text{ mm}$ . The left half of the gap is filled with material of dielectric constant  $\kappa_1 = 21.0$ ; the top of the right half is filled with material of dielectric constant  $\kappa_2 = 42.0$ ; the bottom of the right half is filled with material of dielectric constant  $\kappa_3 = 58.0$ . What is the capacitance? ( $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/(\text{N} \cdot \text{m}^2)$ )



$$C_1 = \frac{\kappa_1 \epsilon_0 A/2}{2d} = \frac{\kappa_1 \epsilon_0 A}{4d} = \frac{21 \times 8.85 \times 10^{-12} \times 10.5 \times 10^{-4}}{4 \times 3.56 \times 10^{-3}} = 13.7 \text{ pF}$$

$$C_2 = \frac{\kappa_2 \epsilon_0 A/2}{d} = \frac{\kappa_2 \epsilon_0 A}{2d} = \frac{42 \times 8.85 \times 10^{-12} \times 10.5 \times 10^{-4}}{7.12 \times 10^{-3}} = 54.8 \text{ pF}$$


$$C_3 = \frac{\kappa_3 \epsilon_0 A/2}{d} = \frac{\kappa_3 \epsilon_0 A}{2d} = \frac{58 \times 8.85 \times 10^{-12} \times 10.5 \times 10^{-4}}{7.12 \times 10^{-3}} = 75.7 \text{ pF}$$

$C_2$  &  $C_3$  are in series  $\rightarrow C_{23} = \frac{C_2 \times C_3}{C_2 + C_3} = \frac{54.8 \times 75.7}{54.8 + 75.7} \text{ pF} = 31.8 \text{ pF}$

$C_1$  &  $C_{23}$  are in parallel  $\rightarrow C_{123} = C_1 + C_{23} = 13.7 + 31.8 = 45.5 \text{ pF}$

$$C_{123} = 45.5 \times 10^{-12} \text{ F} = 4.55 \times 10^{-11} \text{ F}$$

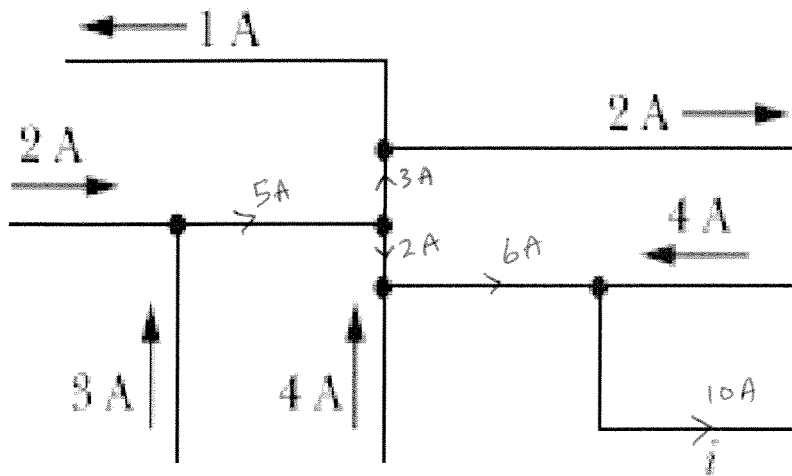6. The figure here shows a portion of a circuit. What is the current  $i$  in the lower right-hand wire? (Include the direction)



$$E_s = -\frac{\partial V}{\partial s}$$

7. What is the electric field in unit vector notation at the point  $(3\mathbf{i} - 6\mathbf{j} + \mathbf{k})$  m if the electric potential is given by  $V = 3x^3yz$ , where  $V$  is in volts and  $x$ ,  $y$ , and  $z$  are in meters?

$$E_x = -\frac{\partial V}{\partial x} = -\frac{\partial}{\partial x}(3x^3yz) = -9x^2yz = -9(3^2)(-6)(1) = 486$$

$$E_y = -\frac{\partial V}{\partial y} = -\frac{\partial}{\partial y}(3x^3yz) = -3x^3z = -3(3)^3(1) = -81$$

$$E_z = -\frac{\partial V}{\partial z} = -\frac{\partial}{\partial z}(3x^3yz) = -3x^3y = -3(3)^3(-6) = 486$$

$$\mathbf{E} = (486\mathbf{i} - 81\mathbf{j} + 486\mathbf{k}) \text{ V/m}$$