

P 2.12. Find v_o and v_g in the circuit in Fig. P2.12.

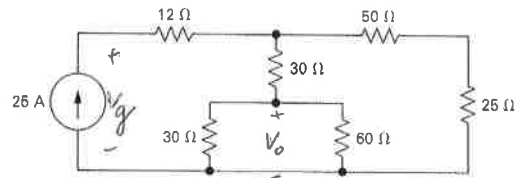


Figure P2.12

P 2.13. Find i_o and i_g in the circuit in Fig. P2.13.

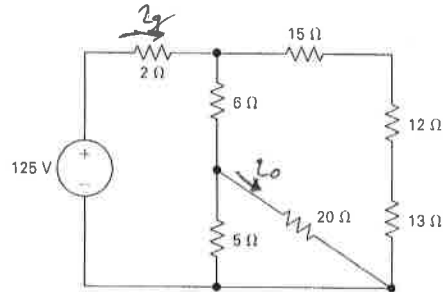


Figure P2.13

P 2.14. For the circuit in Fig. P2.14, calculate (a) i_o and (b) the power dissipated in the 10 Ω resistor.

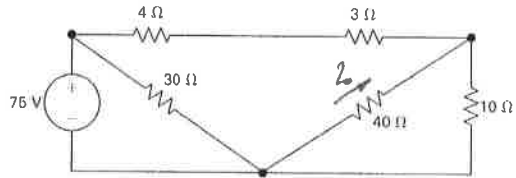


Figure P2.14

P 2.15. The current in the 9 Ω resistor in the circuit in Fig. P2.15 is 1 A, as shown.

- (a) Find v_g .
- (b) Find the power dissipated in the 20 Ω resistor.

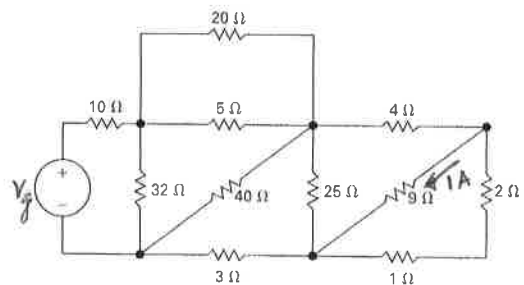


Figure P2.15

Nilsson / Riedel, Intro ckt for Electrical & Computer Eng.